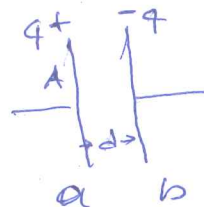


# Capacitance and Dielectrics

## Capacitance


$$C = \frac{q}{V_{ab}}$$

$$V_{ab} = \int_a^b \vec{E} \cdot d\vec{e}$$



Parallel Plate Capacitor:  $C = \frac{\epsilon_0 A}{d}$


## Capacitance in series

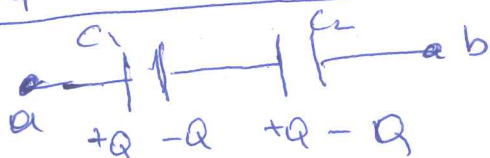

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$

$$Q = C_1 \Delta V_1 = C_2 \Delta V_2 = C_{eq} \cdot V_{ab}$$

## Capacitance in parallel

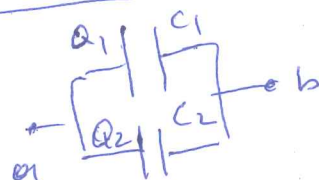

$$C_{eq} = C_1 + C_2 + C_3 + \dots$$


$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2} = V_{ab}$$

$$\frac{Q_1 + Q_2}{C_1 + C_2} = V_{ab}$$
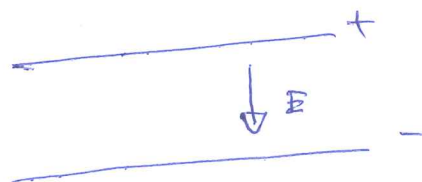
## Energy in a capacitor

$$U = \frac{Q^2}{2C} = \frac{1}{2} CV^2 = \frac{1}{2} QV$$

$$\text{energy density} = \frac{U}{\text{volume}} = \frac{1}{2} \epsilon_0 E^2$$




## Dielectrics


$$C = K \cdot C_0 = K \epsilon_0 \frac{A}{d}$$

$$E = \frac{E_0}{K}$$
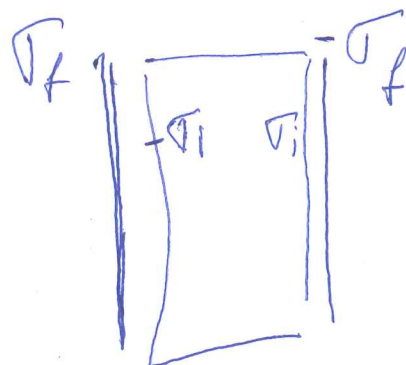
$$\sigma_i = \sigma_{free} \left( \frac{K-1}{K} \right)$$



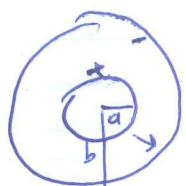4. An air-filled spherical capacitor is constructed with inner- and outer-shell radii of 7.00 cm and 14.0 cm, respectively. (a) Calculate the capacitance of the device. (b) What potential difference between the spheres results in a  $4.00\text{-}\mu\text{C}$  charge on the capacitor?



$$E = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$|\Delta V| = \int_a^b \frac{Q}{4\pi\epsilon_0 r^2} dr = \frac{Q}{4\pi\epsilon_0} \left( \frac{1}{a} - \frac{1}{b} \right)$$

$$C = \frac{Q}{\Delta V} = \frac{1}{\frac{1}{4\pi\epsilon_0} \left( \frac{1}{a} - \frac{1}{b} \right)} = \frac{4\pi\epsilon_0 ab}{(b-a)} = \frac{ab}{k(b-a)}$$

$$(a) \quad C = \frac{(0.07)(0.14)}{8.99 \times 10^9 \times (0.14 - 0.07)}$$


$$C = 15.6 \times 10^{-12} \text{ F}$$

$$(b) \quad C = \frac{Q}{\Delta V} \Rightarrow \Delta V = \frac{Q}{C}$$

$$\Delta V = \frac{4 \times 10^{-6} \text{ C}}{15.6 \times 10^{-12} \text{ F}} = 2.57 \times 10^5 \text{ V}$$

$$\Delta V = 257 \text{ kV}$$

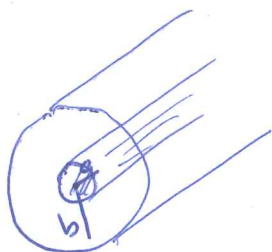5. A 50.0-m length of coaxial cable has an inner conductor that has a diameter of 2.58 mm and carries a charge of  $8.10 \mu\text{C}$ . The surrounding conductor has an inner diameter of 7.27 mm and a charge of  $-8.10 \mu\text{C}$ . Assume the region between the conductors is air. (a) What is the capacitance of this cable? (b) What is the potential difference between the two conductors?



$$E \cdot 2\pi r L = \frac{Q}{\epsilon_0}$$

$$E = \frac{Q}{2\pi\epsilon_0 r L} = \frac{Q/L}{2\pi\epsilon_0 r}$$

$$E = \frac{2kQ}{Lr}$$


$$\Delta V = \int_a^b \frac{2kQ}{Lr} dr = \frac{2kQ}{L} \ln\left(\frac{b}{a}\right)$$

$$C = \frac{Q}{\Delta V} = \frac{L}{2k \ln(b/a)}$$

$$(a) \quad C = \frac{8.10 \times 10^{-6} \text{ C}}{\Delta V} = \frac{50 \text{ m}}{2 \times 8.99 \times 10^9 \times \ln\left(\frac{7.27}{2.58}\right)}$$

$$C = 2.68 \times 10^{-9} \text{ F}$$

9. An air-filled capacitor consists of two parallel plates, each with an area of  $7.60 \text{ cm}^2$ , separated by a distance of  $1.80 \text{ mm}$ . A  $20.0\text{-V}$  potential difference is applied to these plates. Calculate (a) the electric field between the plates, (b) the surface charge density, (c) the capacitance, and (d) the charge on each plate.

  $A = 7.60 \text{ cm}^2 = 7.60 \times 10^{-4} \text{ m}^2$   
 $\Delta V = 20 \text{ V}$   
(a)  $E = \frac{\Delta V}{d} = \frac{20 \text{ V}}{1.80 \times 10^{-3} \text{ m}} = 1.11 \times 10^4 \frac{\text{V}}{\text{m}}$


(b)  $\sigma = \frac{\text{charge}}{\text{area}} = \epsilon_0 E$ , as  $E = \frac{\sigma}{\epsilon_0}$  between plates

$$\sigma = (8.854 \times 10^{-12}) \cdot (1.11 \times 10^4)$$

$$\sigma = 9.83 \times 10^{-8} \frac{\text{C}}{\text{m}^2}$$

$$= 98.3 \frac{\text{nC}}{\text{m}^2}$$

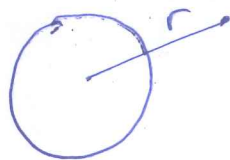11. An isolated, charged conducting sphere of radius 12.0 cm creates an electric field of  $4.90 \times 10^4 \text{ N/C}$  at a distance 21.0 cm from its center. (a) What is its surface charge density? (b) What is its capacitance?



$$r > R$$

$$E = \frac{kQ}{r^2}$$

$$(a) \quad Q = \frac{Er^2}{k}$$

$$Q = \frac{4.90 \times 10^4 \cdot (0.21)^2}{(8.99 \times 10^9)}$$

$$Q = 0.240 \times 10^{-6} \text{ C}$$

$$\sigma = \frac{Q}{\text{area}} = \frac{0.240 \times 10^{-6} \text{ C}}{4 \cdot \pi (0.12)^2} = 1.33 \times 10^{-6} \frac{\text{C}}{\text{m}^2}$$

$$(b) \quad C = \frac{Q}{V} = \frac{Q}{\frac{Q}{4\pi\epsilon_0 r}} = 4\pi\epsilon_0 r$$


$$C = 4\pi (8.854 \times 10^{-12}) \cdot (0.120 \text{ m})$$

$$C = 13.3 \times 10^{-12} \text{ F}$$

$$C = 13.3 \text{ pF}$$



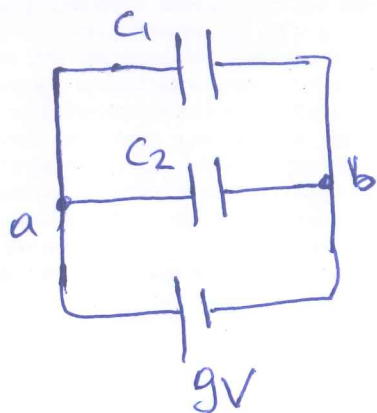13. Two capacitors,  $C_1 = 5.00 \mu\text{F}$  and  $C_2 = 12.0 \mu\text{F}$ , are connected in parallel, and the resulting combination is connected to a 9.00-V battery. Find (a) the equivalent capacitance of the combination, (b) the potential difference across each capacitor, and (c) the charge stored on each capacitor.



$$\begin{aligned} \text{(a)} \quad C_{eq} &= C_1 + C_2 \\ &= 5 \mu\text{F} + 12 \mu\text{F} \\ C_{eq} &= 17 \mu\text{F} \end{aligned}$$


b) They are connected to the same potential  
 $\Delta V = 9.00 \text{ volt}$

$$\begin{aligned} \text{c)} \quad C_1 &= \frac{Q_1}{\Delta V} \Rightarrow Q_1 = C_1 \cdot \Delta V \\ &= 5 \mu\text{F} \cdot 9 \text{ volt} \\ \boxed{Q_1 &= 45 \mu\text{C}} \end{aligned}$$

$$\begin{aligned} Q_2 &= C_2 \cdot \Delta V \\ &= 12 \mu\text{F} \cdot 9 \end{aligned}$$

$$Q_2 = 108 \mu\text{C}$$

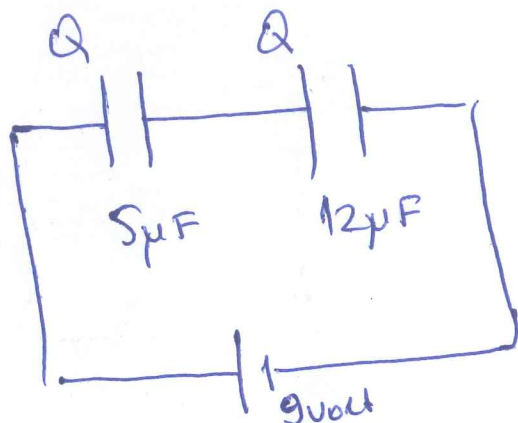14. What If? The two capacitors of Problem 13 ( $C_1 = 5.00 \mu\text{F}$  and  $C_2 = 12.0 \mu\text{F}$ ) are now connected in series and to a 9.00-V battery. Find (a) the equivalent capacitance of the combination, (b) the potential difference across each capacitor, and (c) the charge on each capacitor.



$$(a) \quad \frac{1}{C} = \frac{1}{5} + \frac{1}{12} = \frac{17}{60}$$

$$C_{eq} = \frac{60}{17} \mu\text{F}$$

$$(b) \quad Q = C_{eq} \cdot \Delta V = \frac{60}{17} \cdot 9 \mu\text{C}$$

$$\Delta V_1 = \frac{Q}{C_1} = \frac{\frac{60 \cdot 9}{17} \mu\text{C}}{5 \mu\text{F}} = \frac{12 \cdot 9}{17} \text{ volt}$$

$$V_1 = 6.35 \text{ volt}$$

$$\Delta V_2 = \frac{Q}{C_2} = \frac{\frac{60 \cdot 9}{17}}{12} = \frac{5 \cdot 9}{17} \text{ volt}$$

$$\Delta V_2 = 2.65 \text{ volt}$$

$$\text{or } \Delta V_2 = 9 - \Delta V_1$$

$$(c) \quad Q = \frac{60 \cdot 9}{17} \mu\text{C} = 31.8 \mu\text{C}$$

19. For the system of four capacitors shown in Figure P26.19, find (a) the equivalent capacitance of the system, (b) the charge on each capacitor, and (c) the potential difference across each capacitor.



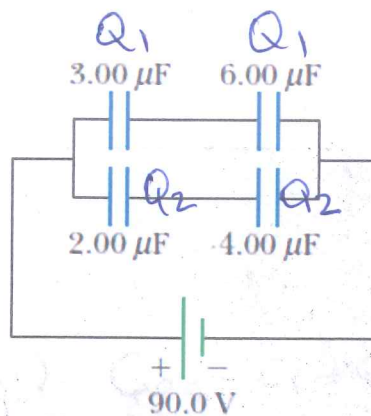


Figure P26.19

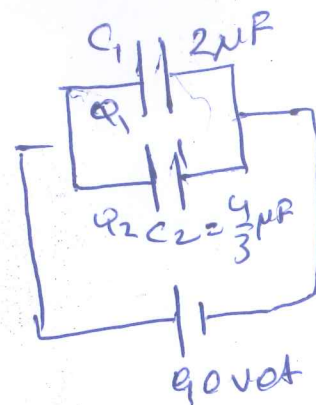

|||

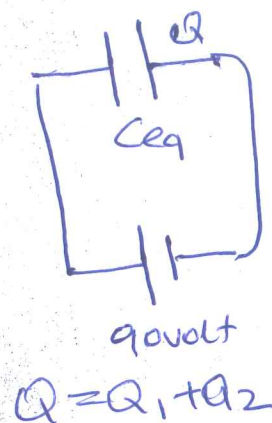

(a)  $\frac{1}{C_1} = \frac{1}{3} + \frac{1}{6} = \frac{3}{6}$

$C_1 = 2 \mu F$

$\frac{1}{C_2} = \frac{1}{2} + \frac{1}{4} = \frac{3}{4}$

$C_2 = \frac{4}{3} \mu F$

$C_{eq} = C_1 + C_2 = 2 + \frac{4}{3} = \frac{10}{3} \mu F$

(b)  $Q_1 = C_1 \cdot 90 = 180 \mu C$

$Q_2 = C_2 \cdot 90 = \frac{4}{3} \cdot 90 \mu C = 120 \mu C$

charge on 3 and 6  $\mu F$  are 180  $\mu C$

charge on 2 and 4  $\mu F$  are 120  $\mu C$

(c)  $\Delta V_{3 \mu F} = \frac{Q_1}{C} = \frac{180 \mu C}{3 \mu F} = 60 \text{ volt}$

$\Delta V_{6 \mu F} = \frac{Q_1}{C} = \frac{180 \mu C}{6 \mu F} = 30 \text{ volt}$

$\Delta V_{2 \mu F} = \frac{Q_2}{C} = \frac{120 \mu C}{2 \mu F} = 60 \text{ volt}$ ,  $\Delta V_{4 \mu F} = \frac{120 \mu C}{4 \mu F} = 30 \text{ volt}$



22. (a) Find the equivalent capacitance between points  $a$  and  $b$  for the group of capacitors connected as shown in Figure P26.22. Take  $C_1 = 5.00 \mu\text{F}$ ,  $C_2 = 10.0 \mu\text{F}$ , and  $C_3 = 2.00 \mu\text{F}$ . (b) What charge is stored on  $C_3$  if the potential difference between points  $a$  and  $b$  is  $60.0 \text{ V}$ ?


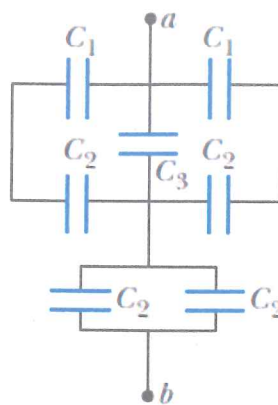


Figure P26.22

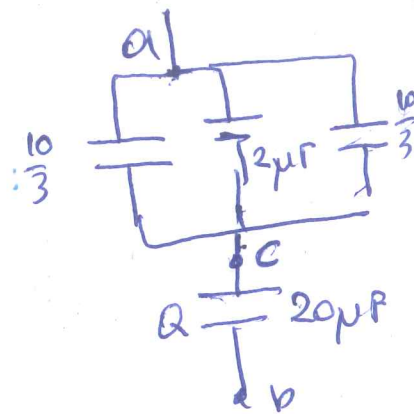

$C_1 + C_2$  in series

$$\frac{1}{C_{eq1}} = \frac{1}{5} + \frac{1}{10} = \frac{3}{10}$$

$$C_{eq1} = \frac{10}{3} \mu\text{F}$$

2  $C_2$ 's are parallel

$$C_{eq2} = 2C_2 = 20 \mu\text{F}$$

$$C_{top} = \frac{10}{3} + 2 + \frac{10}{3} = \frac{26}{3}$$

$$C_{bot} = 20 \mu\text{F}$$



$$\frac{1}{C_{eq}} = \frac{1}{20} + \frac{3}{26} = \frac{26 + 3 \cdot 20}{20 \cdot 26}$$

$$C_{eq} = \frac{20 \cdot 26}{26 + 3 \cdot 20} = 6.05 \mu\text{F}$$

$$Q = C_{eq} \Delta V = 6.05 \times 60 = 363 \mu\text{C}$$

$$|\Delta V_{ac}| = \frac{363 \mu\text{C}}{\frac{26}{3} \mu\text{F}} = 41.9$$

$$Q_3 = |\Delta V_{ac}| \cdot 2 \mu\text{F} = 41.9 \times 2.00 \mu\text{F} = 83.7 \mu\text{C}$$

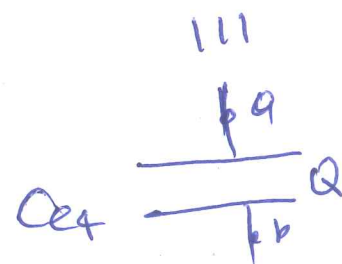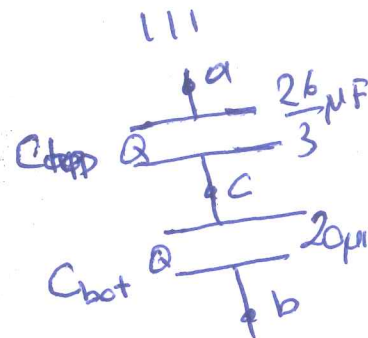

23. Four capacitors are connected as shown in Figure P26.23. (a) Find the equivalent capacitance between points  $a$  and  $b$ . (b) Calculate the charge on each capacitor, taking  $\Delta V_{ab} = 15.0 \text{ V}$ .


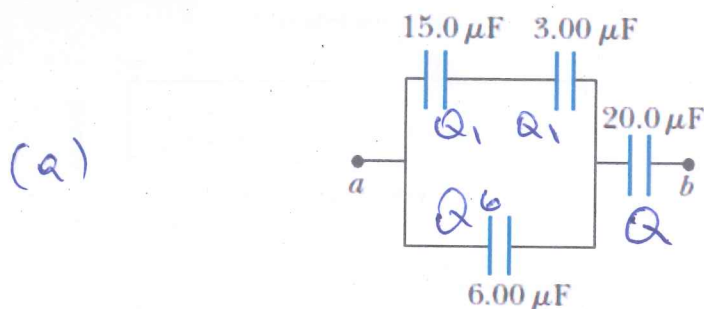


Figure P26.23

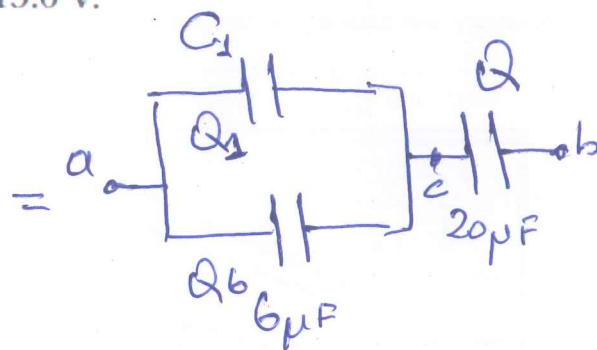


$$\frac{1}{C_2} = \frac{1}{15} + \frac{1}{3} = \frac{6}{15}$$

$$C_2 = \frac{15}{6} \mu\text{F}$$

$$C_2 = C_1 + 6 \mu\text{F} = 6 + \frac{15}{6} = \frac{51}{6} \mu\text{F}$$

$$\frac{1}{C_{eq}} = \frac{6}{51} + \frac{1}{20}$$
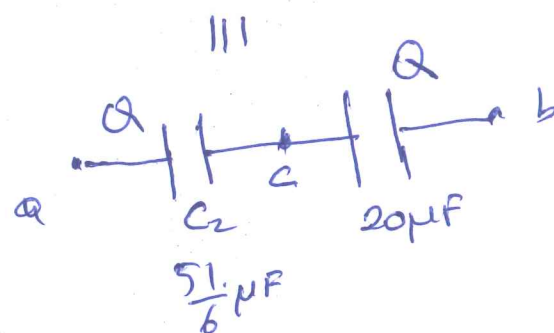
$$C_{eq} = \frac{120 + 51}{51 \cdot 20} \Rightarrow C_{eq} = \frac{51 \cdot 20}{171} = 5.96 \mu\text{F}$$



(b)  $Q = C_{eq} \cdot 150 = 89.5 \mu\text{C}$  charge on  $20.0 \mu\text{F}$

$$V_{ac} = \frac{Q}{C_2} = \frac{89.5}{51/6} = 10.5 \text{ volt}$$

$$Q_1 = C_1 \cdot V_{ac} = \frac{15}{6} \cdot 10.5 = 26.3 \mu\text{C}$$

charge on  
15 μF  
and 3 μF

$$Q_6 = 6 \mu\text{C} \cdot 10.5 \text{ volt} = 63.2 \mu\text{C}$$

charge  
on 6.00 μF

24. Consider the circuit shown in Figure P26.24, where  $C_1 = 6.00 \mu\text{F}$ ,  $C_2 = 3.00 \mu\text{F}$ , and  $\Delta V = 20.0 \text{ V}$ . Capacitor  $C_1$

is first charged by closing switch  $S_1$ . Switch  $S_1$  is then opened, and the charged capacitor is connected to the uncharged capacitor by closing  $S_2$ . Calculate (a) the initial charge acquired by  $C_1$  and (b) the final charge on each capacitor.


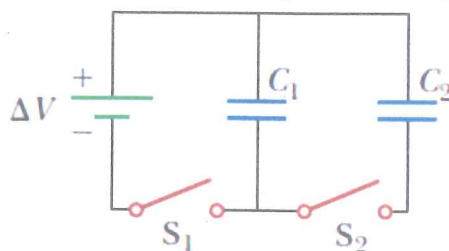



Figure P26.24

(a) initially

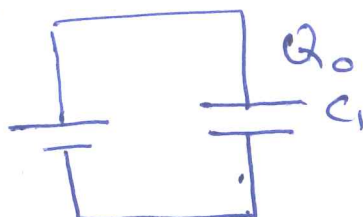

$$Q_0 = C_1 V = 20 \cdot 6 \mu\text{F} = 120 \mu\text{C}$$

(b)

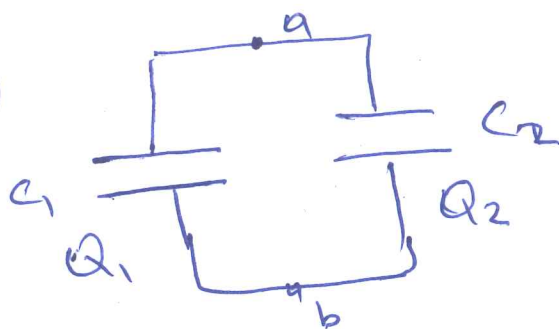

$$Q_1 + Q_2 = Q_0$$

$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2} = \Delta V$$

$$Q_2 + Q_1 = C_1 \Delta V + C_2 \Delta V$$

$$Q_0 = (C_1 + C_2) \Delta V$$

$$\Delta V = \frac{Q_0}{C_1 + C_2}$$

$$Q_1 = C_1 \cdot \frac{Q_0}{C_1 + C_2} = \frac{2}{3} \cdot 120 \mu\text{C} = 80 \mu\text{C}$$

$$Q_2 = C_2 \cdot \frac{Q_0}{C_1 + C_2} = \frac{1}{3} \cdot 120 \mu\text{C} = 40 \mu\text{C}$$

32. (a) A  $3.00\text{-}\mu\text{F}$  capacitor is connected to a  $12.0\text{-V}$  battery.


**W** How much energy is stored in the capacitor? (b) Had the capacitor been connected to a  $6.00\text{-V}$  battery, how much energy would have been stored?

$$\begin{aligned} \text{(a)} \quad U &= \frac{1}{2} C V^2 = \frac{1}{2} (3 \times 10^{-6}) \cdot (12)^2 \\ &= 216 \times 10^{-6} \text{ J} \\ &= 216 \mu\text{J} \end{aligned}$$

$$\begin{aligned} \text{(b)} \quad U &= \frac{1}{2} C \cdot V^2 = \frac{1}{2} (3 \times 10^{-6}) \cdot (6)^2 \\ &= 54 \times 10^{-6} \text{ J} \\ &= 54 \mu\text{J} \end{aligned}$$



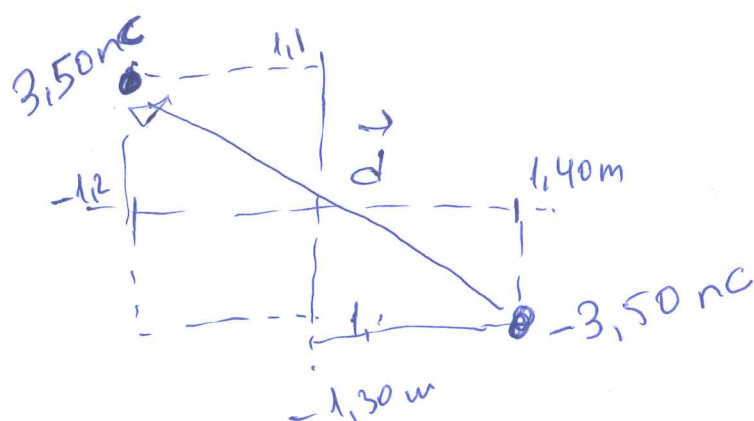- 50.** A small, rigid object carries positive and negative **M** 3.50-nC charges. It is oriented so that the positive charge has coordinates (-1.20 mm, 1.10 mm) and the negative charge is at the point (1.40 mm, -1.30 mm). (a) Find the electric dipole moment of the object. The object is placed in an electric field  $\vec{E} = (7.80 \times 10^3 \hat{i} - 4.90 \times 10^3 \hat{j})$  N/C. (b) Find the torque acting on the object. (c) Find the potential energy of the object-field system when the object is in this orientation. (d) Assuming the orientation of the object can change, find the difference between the maximum and minimum potential energies of the system.



(a) Displacement vector from (-) to (+)

$$\vec{d} = [-1.20 \hat{i} + 1.10 \hat{j} - (1.40 \hat{i} - 1.30 \hat{j})] \text{ mm}$$

$$\vec{d} = [-2.60 \hat{i} + 2.40 \hat{j}] \text{ mm}$$

$$\vec{p} = q \vec{d} = 3.50 \times 10^{-9} [-2.60 \hat{i} + 2.40 \hat{j}] \times 10^{-3} \text{ m}$$

$$\vec{p} = (-9.10 \hat{i} + 8.40 \hat{j}) \times 10^{-12} \text{ C m}$$

b)  $\vec{\tau} = \vec{p} \times \vec{E} = 10^{-12} (-9.10 \hat{i} + 8.40 \hat{j}) \times (7.80 \times 10^3 \hat{i} - 4.90 \times 10^3 \hat{j})$

$$\vec{\tau} = (9.10 \cdot 4.90 \hat{k} - 8.40 \cdot 7.80 \hat{k}) \times 10^{-12}$$

$$\vec{\tau} = (-2.09 \cdot 10^{-8} \hat{k}) \text{ Nm}$$



$$c) \quad U = -\vec{p} \cdot \vec{E}$$

$$= -(-9,10\hat{i} + 8,40\hat{j}) \cdot (7,80\hat{i} - 4,90\hat{j}) \cdot 10^{-9} \text{ Nm}$$

$$U = (9,10 \cdot 7,80 + 8,40 \cdot 4,90) \cdot 10^{-9} \text{ J}$$

$$U = 112 \times 10^{-9} \text{ J} = 112 \text{ nJ}$$

$$d) \quad |\vec{p}| = \sqrt{9,10^2 + 8,40^2} \times 10^{-12} \text{ cm} = 12,4 \times 10^{-12} \text{ cm}$$

$$|\vec{E}| = \sqrt{(7,80)^2 + (4,90)^2} \times 10^3 \frac{\text{N}}{\text{C}} = 9,21 \times 10^3 \text{ N/C}$$

$$U_{\min} = -|\vec{p}| |\vec{E}| = -114 \times 10^{-9} \text{ Nm} = -114 \text{ nJ}$$

$$U_{\max} = |\vec{p}| |\vec{E}| = 114 \text{ nJ}$$

$$\Delta U = U_{\max} - U_{\min} = 228 \text{ nJ}$$

59. A parallel-plate capacitor is constructed using a dielectric material whose dielectric constant is 3.00 and whose dielectric strength is  $2.00 \times 10^8 \text{ V/m}$ . The desired capacitance is  $0.250 \mu\text{F}$ , and the capacitor must withstand a maximum potential difference of 4.00 kV. Find the minimum area of the capacitor plates.

$$E_{\text{max}} = 2 \times 10^8 \frac{\text{V}}{\text{m}} = \frac{\Delta V}{d_{\text{min}}}$$

$$d_{\text{min}} = \frac{\Delta V}{2 \times 10^8 \frac{\text{V}}{\text{m}}} = \frac{4000 \text{ V}}{2 \times 10^8 \frac{\text{V}}{\text{m}}} = 2 \times 10^{-5} \text{ m}$$

$$C = K \frac{\epsilon_0 A}{d}$$

$$A = \frac{C d}{K \epsilon_0} = \frac{0.250 \times 10^{-6} \cdot 2 \times 10^{-5}}{3 \cdot 8.854 \times 10^{-12}} = 0.188 \text{ m}^2$$

63. A  $10.0\text{-}\mu\text{F}$  capacitor is charged to  $15.0\text{ V}$ . It is next connected in series with an uncharged  $5.00\text{-}\mu\text{F}$  capacitor. The series combination is finally connected across a  $50.0\text{-V}$  battery as diagrammed in Figure P26.63. Find the new potential differences across the  $5.00\text{-}\mu\text{F}$  and  $10.0\text{-}\mu\text{F}$  capacitors after the switch is thrown closed.


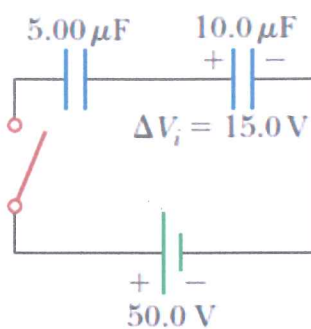


Figure P26.63
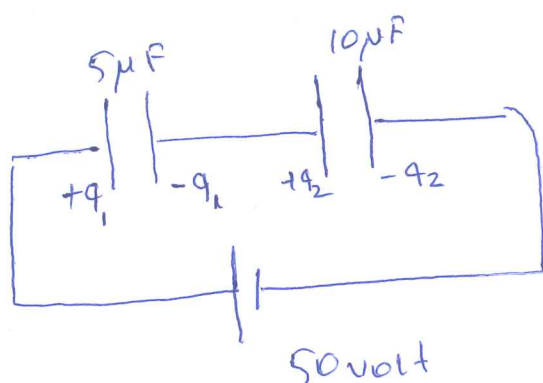
$$q_i = C \cdot \Delta V_i = 10\text{ }\mu\text{F} \cdot 15\text{ V} = 150\text{ }\mu\text{C}$$



$$q_2 - q_1 = +150\text{ }\mu\text{C}$$

$$\Delta V_1 = q_1 / 5\text{ }\mu\text{F}$$

$$\Delta V_2 = q_2 / 10\text{ }\mu\text{F}$$

$$\frac{q_1}{5\text{ }\mu\text{F}} + \frac{q_2}{10\text{ }\mu\text{F}} = 50$$

$$2q_1 + q_2 = 500\text{ }\mu\text{C}$$

$$q_2 - q_1 = 150\text{ }\mu\text{C}$$

$$3q_1 = 350\text{ }\mu\text{C}$$

$$q_1 = \frac{350}{3}\text{ }\mu\text{C}$$

$$q_2 = q_1 + 150\text{ }\mu\text{C}$$

$$q_2 = \frac{800}{3}\text{ }\mu\text{C}$$

$$\Delta V_1 = \frac{q_1}{5\text{ }\mu\text{F}} = \frac{350}{3.5} = \frac{70}{3}\text{ volt}$$

$$\Delta V_2 = \frac{q_2}{10\text{ }\mu\text{F}} = \frac{800}{3.10} = \frac{80}{3}\text{ volt}$$